



Operating Systems & Networks CTEC1704C

Lecture - 6 : Logic Gates & Hardware Memory

Dr. Sameer Jha, SFHEA
Faculty of Computing
De Montfort University Cambodia



Outline

- Logic Gates
- Boolean Operations: AND
- Boolean Operations: OR
- Boolean Operations: NOT
- Boolean Operations: NAND
- Boolean Operations: NOR
- Memory Technologies



Logic gates are the fundamental building blocks in digital electronics.

- Used to perform logical operations based on the inputs provided to it and gives a logical output that can be either high(1) or low(0).
- The operation of logic gates is based on Boolean algebra, or mathematics.
- There are basically seven main types of logic gates that are used to perform various logical operations in digital systems.
- By combining different logic gates, complex operations are performed, and circuits like flip-flops, counters, and processors are designed. In this article, we will see various types of logic gates in detail.
- Logic gates find their uses in our day-to-day lives, such as in the architecture of our telephones, laptops, tablets and memory devices.



Transistors

- A transistor is an on/off switch
 - On allows current to flow through the circuit
 - Off blocks the flow of current
- We can create a **physical** equivalent of the **logical** operations AND/OR/NOT by combining a few transistors





Boolean Operations: AND

- Yields true (binary value 1) if and only if both of its operands are true
- Represented by simple concatenation or the dot operator:

$$A \text{ \textasciitilde\textasciitilde } B = AB$$

- Symbol in a circuit diagram: 

- Truth table:

Inputs		Output
A	B	F = A AND B
0	0	0
0	1	0
1	0	0
1	1	1

Source: https://en.wikipedia.org/wiki/File:NMOS_AND_gate.png



Boolean Operations: OR

- Yields true if either or both of its operands are true
- Represented by the plus sign: $A+B$

- Symbol in a circuit diagram: 

- Truth table:

Inputs		Output
A	B	$F = A \text{ OR } B$
0	0	0
0	1	1
1	0	1
1	1	1




Boolean Operations: NOT

- Inverts the value of its operand
- Represented by the overbar:

$\bar{A}$

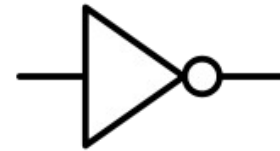- Symbol in a circuit diagram:
- Truth table:



Input	Output
A	F = NOT A
0	1
1	0

NAND: NOT + AND

- We can combine the basic Boolean operations into more complex functions
- For example: NAND
- Symbol in a circuit diagram:
- Truth table:





Inputs		Output
A	B	$F = A \text{ NAND } B$
0	0	1
0	1	1
1	0	1
1	1	0

Source: https://en.wikipedia.org/wiki/File:NMOS_NAND.svg



Combining NAND Gates

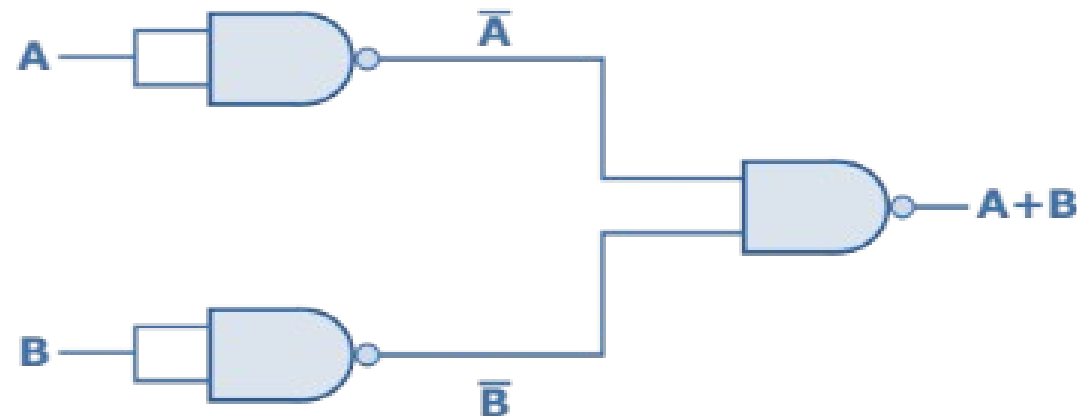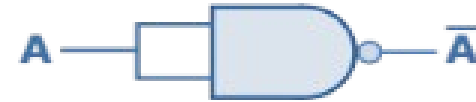- AND, OR, and NOT can be implemented using only NAND Gates
- Great for circuit hardware: only need one type of gate!
- NAND gates are **functionally complete**






NOR gate



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


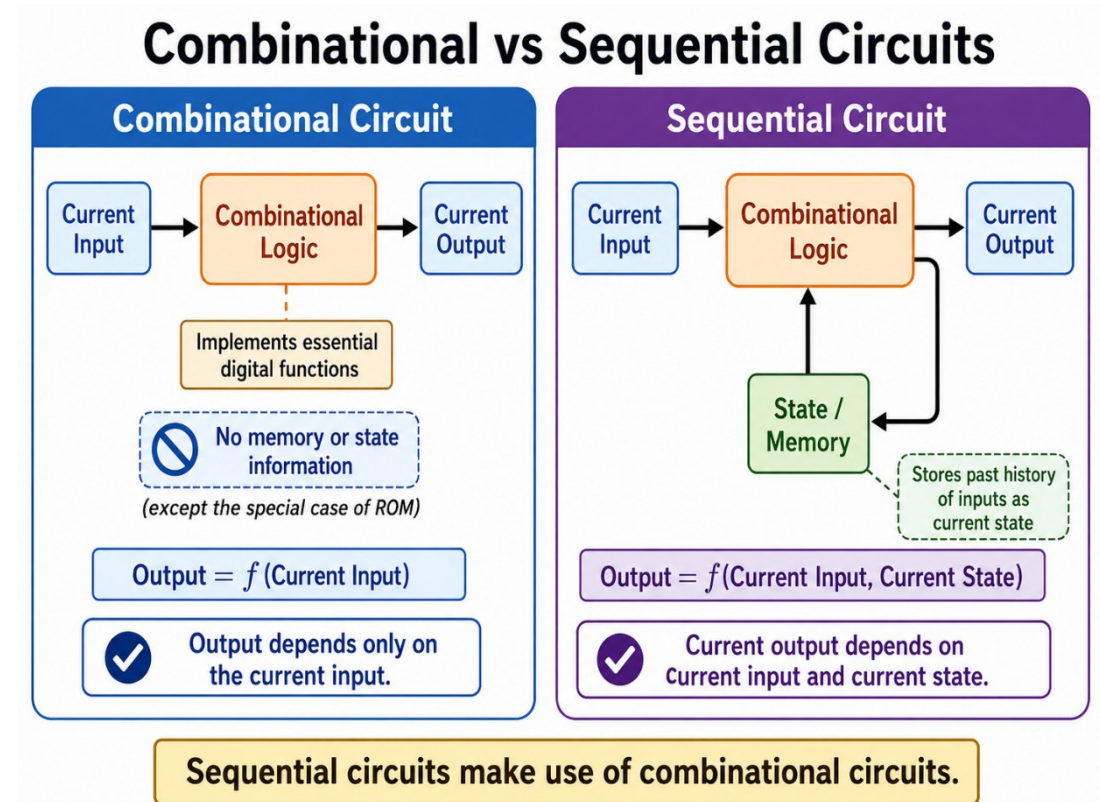
- Combinational circuits depend only on current input
 - cannot store state information!
- Sequential circuits:
 - Current output depends not only on the current input, but also on the past history of inputs
 - Uses combinational circuits as building blocks
- Useful sequential circuits:
 - Flip-flops





Flip-Flops

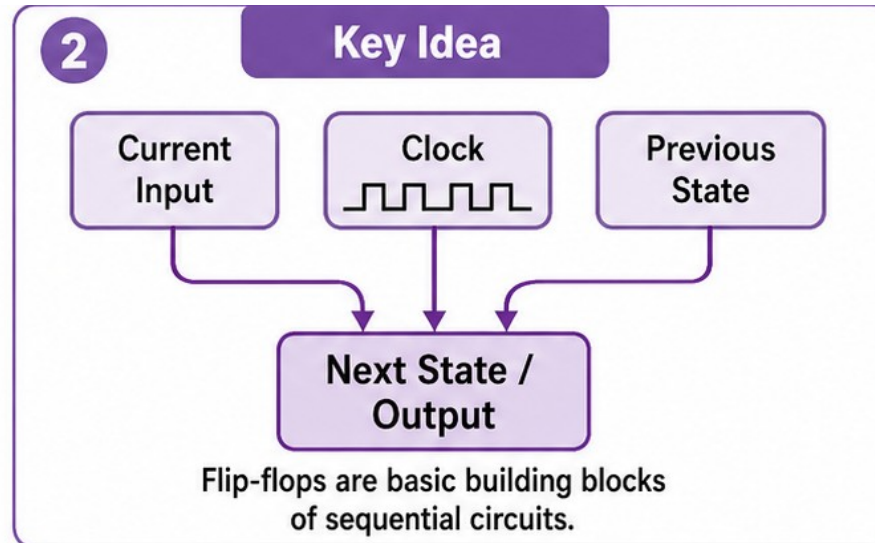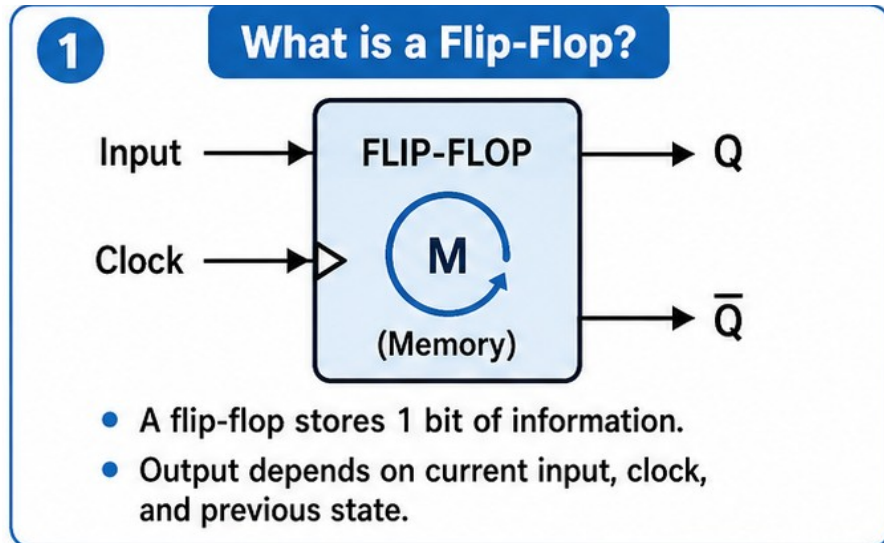
- Simplest form of sequential circuit
- There are a variety of flip-flops, all of which share two properties:
 - The flip-flop is a **bistable** device. It exists in **one of two states** and, in the absence of input, remains in that state. Thus, the flip-flop can function as a **1-bit memory**.
 - The flip-flop has two outputs, which are always the complements of each other.





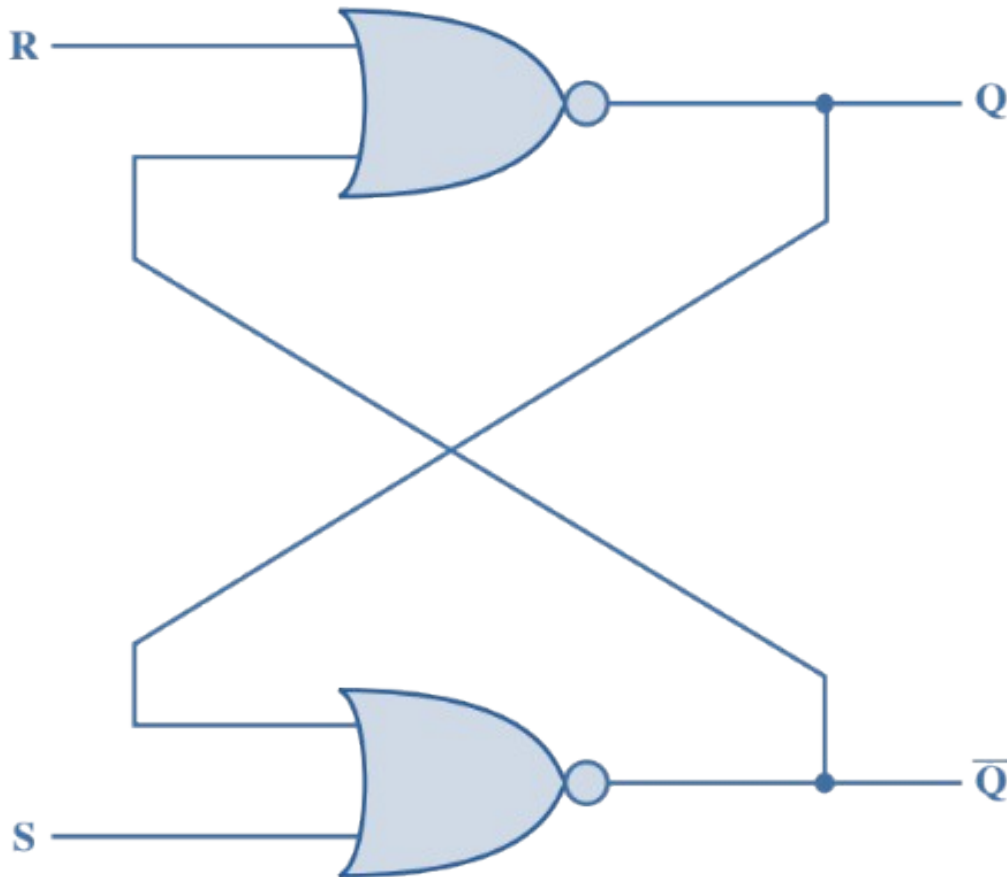Example Flip-Flop: the S-R Latch


- Pair of cross-coupled NOR gates
- Inputs S (set) and R (reset)



S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	-

Not allowed!

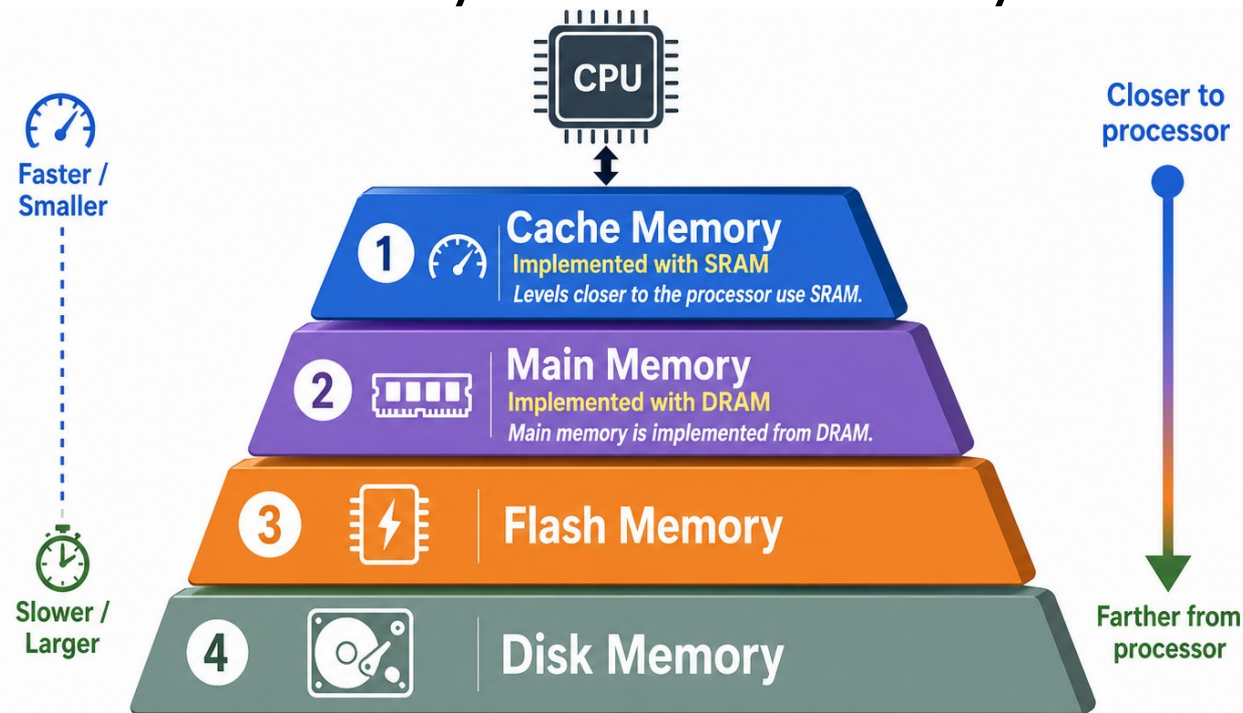- There are four primary technologies used today in memory hierarchies
- Main memory is implemented from DRAM (dynamic random access memory), while levels closer to the processor (caches) use SRAM (static random access memory)
- The Third and Fourth are Flash memory and disk memory.



- SRAMs are simply integrated circuits that are memory arrays with (usually) a single access port that can provide either a read or a write.
- SRAMs have a fixed access time to any datum, though the read and write access times may differ.
- SRAMs typically use six to eight transistors per bit to prevent the information from being disturbed when read



- In a SRAM, as long as power is applied, the value can be kept indefinitely. In a dynamic RAM (DRAM), the value kept in a cell is stored as a charge in a capacitor.
- A single transistor is then used to access this stored charge, either to read the value or to overwrite the charge stored there.
- As DRAMs store the charge on a capacitor, it cannot be kept indefinitely and must periodically be refreshed. That is why this memory structure is called dynamic, in contrast to the static storage in an SRAM cell.





Differences

<u>SRAM</u>	<u>DRAM</u>
1. SRAM has lower access time, so it is faster compared to DRAM.	1. DRAM has higher access time, so it is slower than SRAM.
2. SRAM is costlier than DRAM.	2. DRAM costs less compared to SRAM.
3. SRAM requires constant power supply, which means this type of memory consumes more power.	3. DRAM offers reduced power consumption, due to the fact that the information is stored in the capacitor.
4. Due to complex internal circuitry, less storage capacity is available compared to the same physical size of DRAM memory chip.	4. Due to the small internal circuitry in the one-bit memory cell of DRAM, the large storage capacity is available.
5. SRAM has low packaging density.	5. DRAM has high packaging density.



Flash and disk memory

- Flash memory is a type of electrically erasable programmable read-only memory (EEPROM).
- It is a type of nonvolatile memory that erases data in units called blocks and rewrites data at the byte level
- More on Flash Memory –
- <https://computer.howstuffworks.com/flash-memory.htm>
- What you should know about disk storage
- <https://computer.howstuffworks.com/hard-disk.htm>,
<https://www.youtube.com/watch?v=NtPc0jI21i0>
(interesting)



Thank You!